
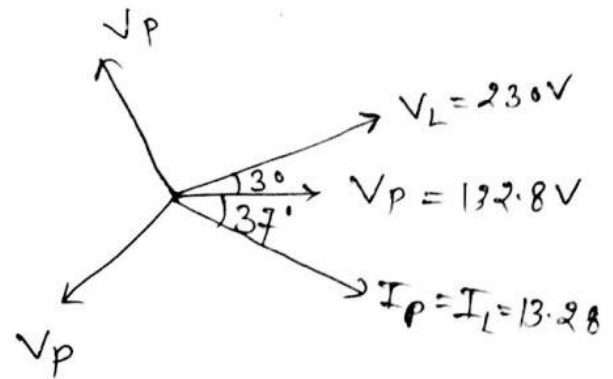


Ques. 5 > A balance star connected load of $(8+j6)\Omega$ per phase is connected to 3 phase, 230V, 50Hz. Supply. Find the line current, power factor, Volt amperes reactive. Draw the phasor Diagram for chkt.

Ans. >

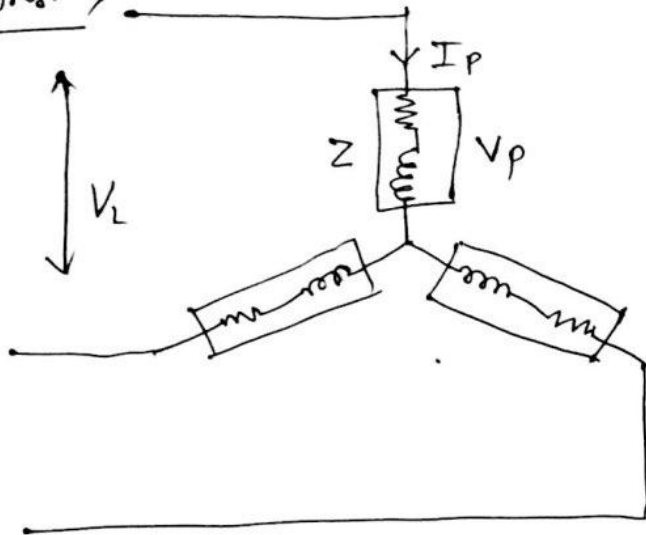

now given $\rightarrow V_L = 230V$
 $Z = 8+j6\Omega$

$$Z = \sqrt{8^2 + 6^2} = 10\Omega$$

$$V_P = V_L / \sqrt{3} = 132.8V$$

now

$$I_P = \frac{V_P}{Z} = \frac{132.8}{10} = 13.28A$$

(i) $I_L = I_P = 13.28A$

(ii) $\cos\phi = R/Z = 0.8$ and $\phi = 36.87^\circ$

(iii) $P = 3 V_P I_P \cos\phi = 3 \times 132.8 \times 13.28 \times 0.8 = 4.232kW$

(iv) $P_R = 3 V_P I_P \sin\phi = 3 \times 132.8 \times 13.28 \times 0.6 = 3.179kVAR$

Ques. 6 > A 3 ϕ balance load draw 10kW Power from a 400V, 3phase, supply at 0.8 lagging power factor. determine (i) line current (ii)


Ans. > $P = 10kW$ $V_L = 400V$ $\cos\phi = 0.8$

$$P = 3 V_P I_P \cos\phi = \sqrt{3} V_L I_L \cos\phi$$

$$\boxed{I_L = 18.04A} \text{ on}$$

Ques. 7 > Prove that Power can be measured by two wattmeter method for star & Delta Connected System.

(i) Star connected system >

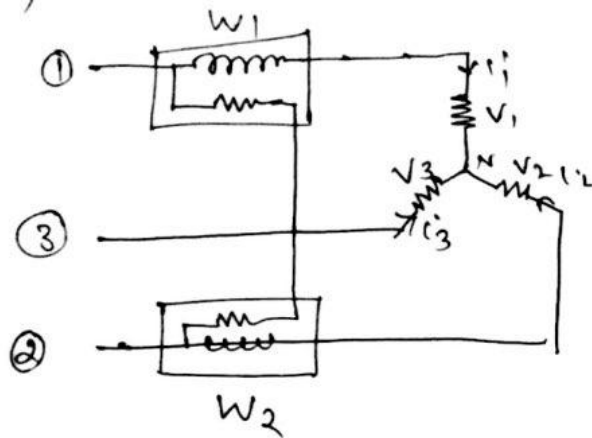

Total Power in star is given by

$$P = V_1 i_1 + V_2 i_2 + V_3 i_3 \quad \text{--- (i)}$$

apply KCL at node N

$$i_1 + i_2 + i_3 = 0$$

$$i_3 = -(i_1 + i_2)$$

Put the value of i_3 in eq. (i)

$$P = V_1 i_1 + V_2 i_2 - V_3 (i_1 + i_2)$$

$$P = i_1 (V_1 - V_3) + i_2 (V_2 - V_3) \quad \text{--- (ii)}$$

* Now for wattmeter reading.

(W₁) → the current coil having current i_1 & pressure coil voltage is $V_{13} = (V_1 - V_3)$ so wattmeter reading is

$$W_1 = i_1 (V_1 - V_3)$$


Similarly $W_2 = i_2 (V_2 - V_3)$

by eq. (ii) total Power is now

$$\boxed{P = W_1 + W_2}$$

So total Power can be measured by two wattmeter Method

(ii) Delta Connected System >

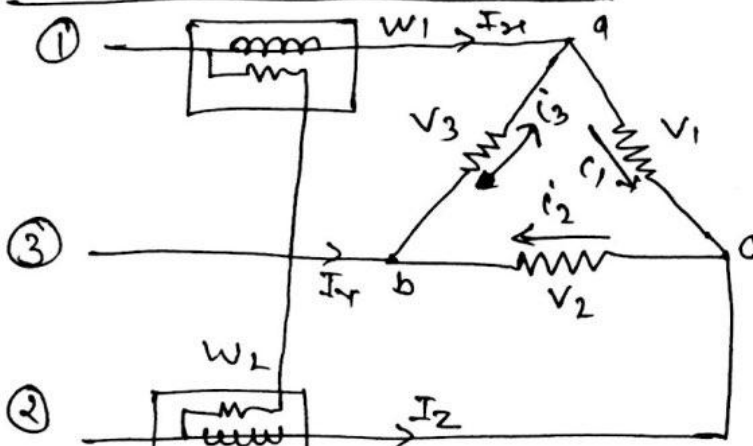

Total Power in Delta Connected System is

$$P = V_1 i_1 + V_2 i_2 + V_3 i_3 \quad \text{--- (i)}$$

apply KVL in loop abcba →

$$V_1 + V_2 + V_3 = 0$$

$$V_1 = -(V_2 + V_3)$$

Put the Value of V_1 in eq. (1)

$$P = V_1 I_1 + V_2 I_2 + V_3 I_3$$

$$= -(V_2 + V_3) I_1 + V_2 I_2 + V_3 I_3$$


$$P = -V_3(I_1 - I_3) + V_2(I_2 - I_1)$$

Comparing with wattmeter reading $\rightarrow$

$$P = W_1 + W_2$$

Ques. 8 > Derive the Expression for power Factor by wattmeter reading.

Ans. >

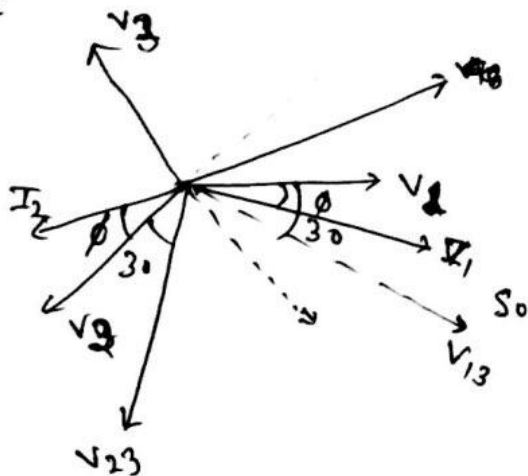

Wattmeter readings are

$$W_1 = I_1 (V_1 - V_3)$$

$$W_2 = I_2 (V_2 - V_3)$$

for inductive load $\rightarrow$

$$W_1 = V_L I_L \cos(30 - \phi)$$

$$W_2 = V_L I_L \cos(30 + \phi)$$

$$\text{now } W_1 + W_2 = V_L I_L \cos(30 - \phi) + V_L I_L \cos(30 + \phi)$$

$$= \sqrt{3} V_L I_L \cos \phi$$

$$W_1 - W_2 = V_L I_L \cos(30 - \phi) - V_L I_L \cos(30 + \phi)$$

$$= V_L I_L [2 \sin 30 \sin \phi]$$

$$= V_L I_L \sin \phi$$

$$\frac{W_1 - W_2}{W_1 + W_2} = \frac{1}{\sqrt{3}} \tan \phi$$

$$\tan \phi = \sqrt{3} \left(\frac{W_1 - W_2}{W_1 + W_2} \right)$$

$$\boxed{\cos \phi = \cos \tan^{-1} \sqrt{3} \left(\frac{W_1 - W_2}{W_1 + W_2} \right)}$$

Ques.1 > Explain Different type of Magnetic Material

Ans. > Magnetic Materials are basically three types

- (i) Paramagnetic Material
- (ii) Diamagnetic Material
- (iii) Ferromagnetic Material

(i) Paramagnetic Materials > The materials which are not strongly attracted by a magnet are known as Paramagnetic material.


Ex. → aluminium, platinum, magnesium.

(ii) Diamagnetic Materials > The materials which are repelled by a magnet such as Zinc, mercury, lead are known as Diamagnetic materials.

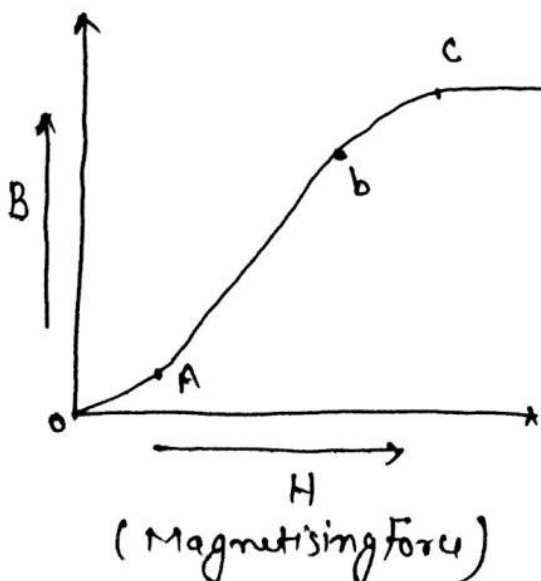(iii) Ferromagnetic Materials > The material which are strongly attracted by a magnet such as Iron, steel, Nickel are known as ferromagnetic materials.

Ques.2 > Explain B-H curve in detail >

Ans. > The Curve Drawn b/w Induction density B and Magnetising Force H is known as B-H curve or magnetising curve.



* in region OA increase in flux density is very small

* in region ab flux density is directly proportional to magnetising force

* in region bc again increase in flux density is very small.


* beyond c there is no change in flux density on increasing the magnetising force this region is known as Magnetic Saturation.

Ques-3 > Explain Ideal & Practical Transformer.


Ans. > For a Ideal Transformer we take following assumption's →

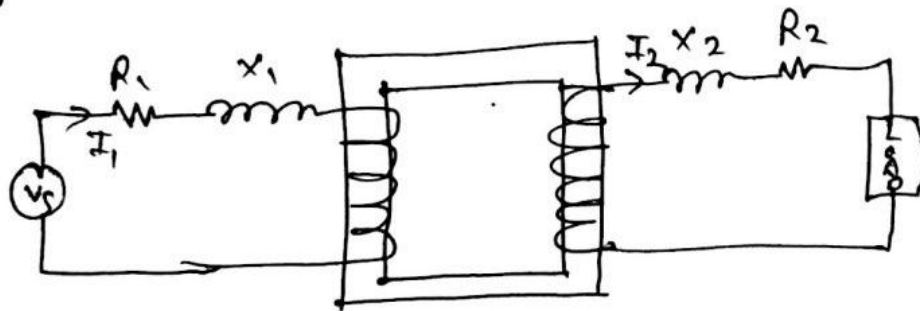- (i) No winding resistance → The primary & Secondary winding's have No resistance.
- (ii) No magnetic leakage → There is No leakage Flux all the flux setup is confined to the core.
- (iii) No Iron loss → There is No Hysteresis and eddy current loss.
- (iv) Zero magnetising current → The Core has Infinite Permeability and zero reluctance.

Practical Transformer > The Transformer which Not follow the assumption of Ideal Transformer is known as practical Transformer



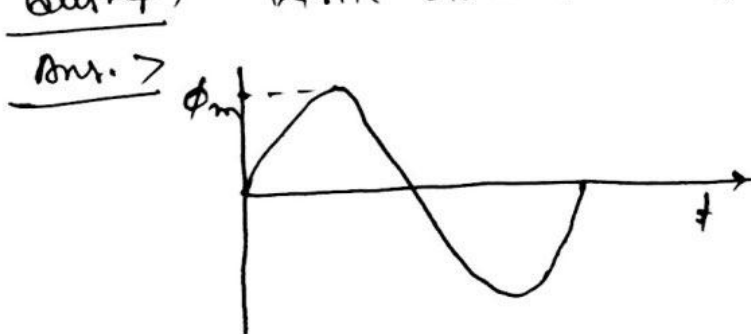Ques-4 > Write down E.m.f. Equation of transformer



* Let flux associated with the core is

$$\phi = \phi_m \sin \omega t$$

* N_1 & N_2 no of turn in primary and secondary winding.

* Now Induced e.m.f in Primary winding

$$\begin{aligned} E_1 &= -N_1 \frac{d\phi}{dt} = -N_1 \omega \phi_m \cos \omega t \\ &= N_1 \omega \phi_m \sin(\omega t - \pi/2) \end{aligned}$$

Similarly

$$E_2 = -N_2 \frac{d\phi}{dt}$$

$$= -N_2 \frac{d}{dt} (\phi_m \sin \omega t)$$

$$= N_2 \omega \phi_m \sin(\omega t - \pi/2)$$

Now ~~primary~~ ^{r.m.s.} value of induced e.m.f.

$$E_1 = \frac{N_1 \phi_m \omega}{\sqrt{2}}$$


$$= \frac{N_1 \phi_m 2\pi f}{\sqrt{2}}$$

$$E_1 = 4.44 f \phi_m N_1 \text{ Volt}$$

$$E_2 = 4.44 f \phi_m N_2 \text{ Volt}$$

Ques 5 > Draw and Explain Equivalent circuit of Transformer.

Ans. >

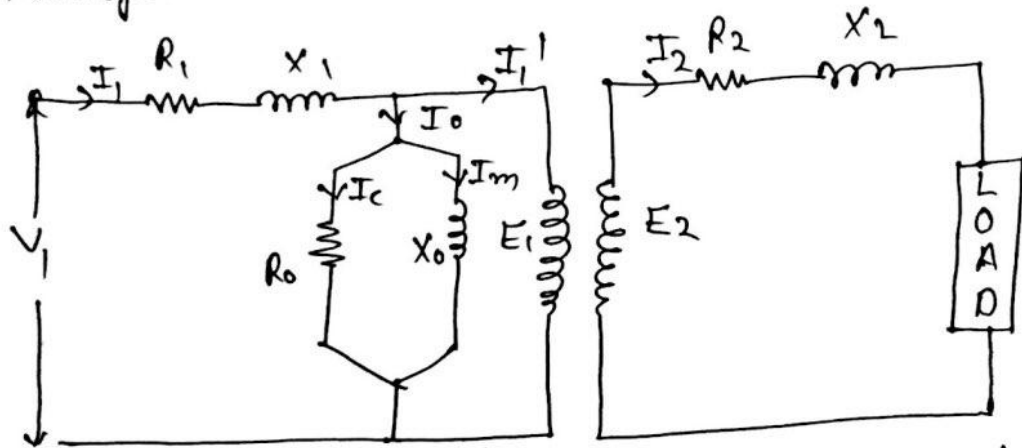

Equivalent ckt of any device can be quite helpful in predetermination of the behavior of the device under various condition of operation.

$R_1, X_1 \rightarrow$ Primary Resistance and Reactance

$R_2, X_2 \rightarrow$ Secondary Resistance and Reactance.

$I_1, I_2 \rightarrow$ Primary & Secondary current

$R_0, X_0 \rightarrow$ No-load parameter of Transformer.

$I_0 \rightarrow$ No-load current

I_1' → Counter balancing current which neutralized the flux produced by secondary current.

$$I_1 = I_0 + I_1'$$

$$N_1 I_1 = N_2 I_2$$

Ques 6 → Explain Different type of losses present in Transformer.

Ans. → There are two types of losses present in Transformer

(i) Copper loss

(ii) Iron loss

Copper loss → Copper loss is basically due to resistance and it takes place in primary & secondary winding.

$$P_c = I_1^2 R_1 + I_2^2 R_2$$

Iron loss → Iron loss is also two types.

(i) Hysteresis loss

(ii) Eddy current loss.

(i) Hysteresis loss → When alternating flux setup in the core the Hysteresis loop is traced out and area under Hysteresis loop represent Hysteresis loss. and it is given by

$$P_h = \eta (B_{max})^n f V \text{ Joule}$$

where η → Hysteresis coefficient

B_{max} → Max. flux density

f → Supply frequency

V → Volume of core.

(ii) Eddy current loss → When variable flux setup in the core the flux linkage with iron core is change due to which a current is

Induced in the core this current is known as Eddy Current and result heating loss which is known as Eddy current loss. and is given by

$$P_e = K_e (B_{max})^2 f^2 t^2 V \text{ Watt}$$

Ques. 7 → What is the efficiency of Transformer. Derive the expression for Max. efficiency.

Ans. 7 → The efficiency of any machine is given by

$$\eta = \frac{\text{output}}{\text{Input}} = \frac{\text{output}}{\text{output} + \text{losses}}$$

for a fixed Input Voltage Iron loss is constant but Copper loss is depend upon Load current

$$\eta = \frac{\text{output}}{\text{output} + \text{Copper loss} + \text{Iron loss}}$$

let $P_o \rightarrow$ output Power at full load

$P_i \rightarrow$ Iron loss

$P_c \rightarrow$ Copper loss at full load

then efficiency at x -load where x is fraction of full load $\rightarrow$

$$\eta = \frac{x P_o}{x P_o + P_i + x^2 P_c}$$

for max. efficiency

$$\frac{d\eta}{dx} = 0 \quad \text{now} \quad \frac{d\eta}{dx} = \frac{(x P_o + x^2 P_c + P_i) P_o - x P_o (1 + 2x P_c)}{(x P_o + P_i + x^2 P_c)^2}$$

$$P_i - x^2 P_c = 0$$

$$x = \sqrt{\frac{P_i}{P_c}}$$

Ques. 8 → In a 25 kVA 2000 V/200 V Transformer
The Iron and Copper losses are 200 W and 400 W respectively calculate the efficiency at half load 0.8 Power Factor lagging, also determine max. efficiency and corresponding load.

Ans. 7 $P_c = 400 \text{ W} = 0.4 \text{ kW}$
 $P_i = 200 \text{ W}$

$$P_o = \frac{1}{2} \times V \times I \times \cos\phi$$

$$= \frac{1}{2} \times 25 \times 0.8$$

$$= 10 \text{ kW}$$

* Copper loss at half load = $\left(\frac{1}{2}\right)^2 \times 400 = 0.1 \text{ kW}$

* efficiency at half load →

$$\% \eta = \frac{10}{10 + 0.1 + 0.2} \times 100 = 97.08\%$$


* for max efficiency $x = \sqrt{\frac{P_i}{P_c}} \Rightarrow$

$$\text{Corresponding load} = 25 \times \sqrt{\frac{P_i}{P_c}} = 17.68 \text{ kVA}$$

$$\text{So max. efficiency} = \frac{17.68}{17.68 + 0.2 + 0.2} = 97.788\%$$

Ques. 9 → What is Auto Transformer. How Conducting Material saved in Auto Transformer.

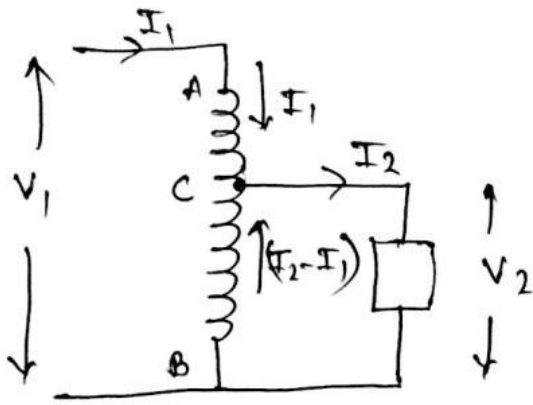Ans. 7 The Auto Transformer has same principal as like conventional two winding transformer the only difference is that in auto transformer primary and secondary windings are Interrelated.



$$\frac{V_2}{V_1} = \frac{E_{BC}}{E_{AB}} = \frac{N_2}{N_1} = \frac{I_1}{I_2} = K$$

Conducting Material → Conducting Material required is Directly Proportional to cross sectional area and length of Conductor so.

Conducting Material in ordinary Transformer
 $C_0 \propto (N_1 I_1 + N_2 I_2)$
 $C_0 \propto 2N_1 I_1$ because $N_1 I_1 = N_2 I_2$

In auto Transformer

$$C_A \propto I_1 (N_1 - N_2) + N_2 (I_2 - I_1)$$

$$C_A \propto 2(N_1 - N_2) I_1$$

now

$$\frac{C_A}{C_0} = \frac{2(N_1 - N_2) I_1}{2N_1 I_1} = 1 - \frac{N_2}{N_1} = 1 - K$$

$$C_A = C_0 (1 - K)$$

Conducting Material Saved.

$$C_0 - C_A = C_0 - C_0 (1 - K)$$

$$= C_0 K$$


$$\text{Saving} = K \times \text{Conducting Material in Ordinary}$$

Ques.10 > Explain Different type of Three phase Transformer Inter Connection.

Ans. > The winding of Three phase Transformer are either connected in star or Delta. According to Primary & Secondary Winding Interconnection there are four method of Interconnection.

- (i) Y-Y (Star-Star) Connection
- (ii) Δ-Δ (Delta-Delta) Connection
- (iii) Y-Δ (Star-Delta) Connection
- (iv) Δ-Y (Delta-Star) Connection

(i). Y-Y (Star-Star) Connection:

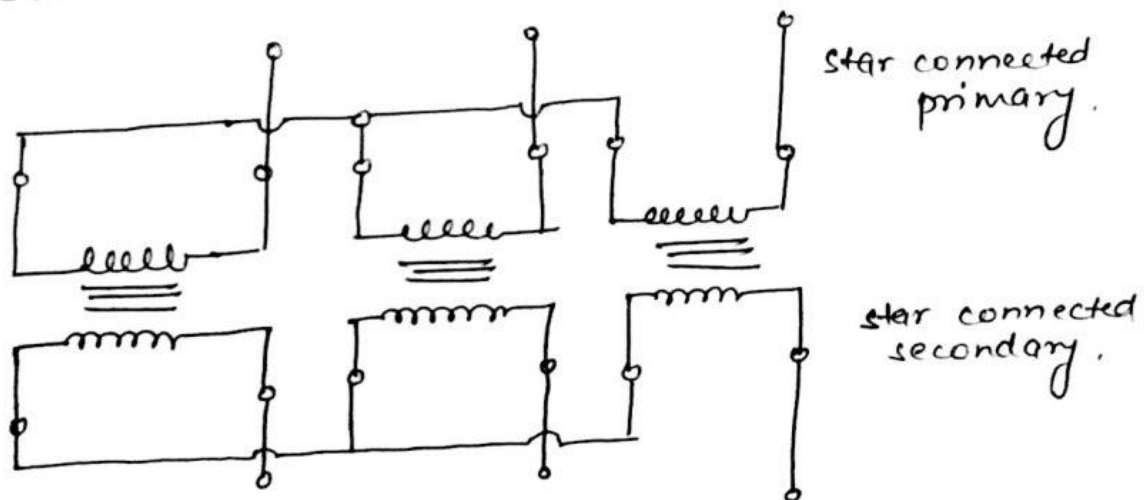


It gives line voltage $\sqrt{3}$ times phase voltage. It is economical for small rating, high voltage transformers as the number of turns per phase and the amount of insulation required is less.

$$\text{Voltage ratio} = \frac{V_{L2}}{V_{L1}} = \frac{\sqrt{3} V_{P2}}{\sqrt{3} V_{P1}} = \frac{N_2}{N_1}$$

$$\text{Current ratio} = \frac{I_{L2}}{I_{L1}} = \frac{I_{P2}}{I_{P1}} = \frac{N_1}{N_2}$$

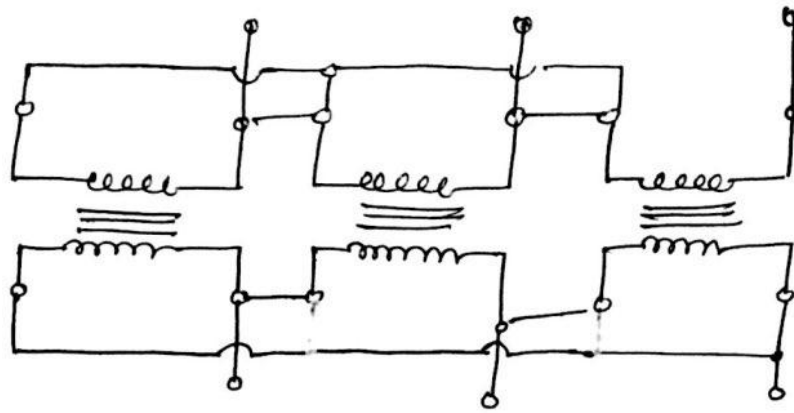(ii). $\Delta-\Delta$ (Delta Delta Connections)



star connected primary


star connected secondary.

This arrangement is generally used in systems which carry large currents on low voltages. The conductor is required of smaller cross section as the phase current is $\frac{1}{\sqrt{3}}$ times the line current.

$$\text{Voltage ratio} = \frac{V_{L2}}{V_{L1}} = \frac{V_{P2}}{V_{P1}} = \frac{N_2}{N_1}$$

$$\text{Current ratio} = \frac{I_{L2}}{I_{L1}} = \frac{\sqrt{3} I_{P2}}{\sqrt{3} I_{P1}} = \frac{N_1}{N_2}$$

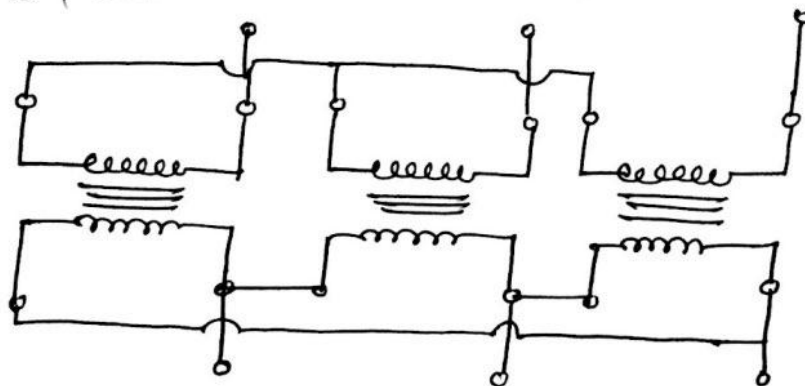(iii). $Y-\Delta$ (star Delta Connection):



star connected primary


Delta connected primary.

Such connections are used principally where the voltage is to be stepped down. The neutral of the primary winding is earthed.

$$\text{Voltage ratio} = \frac{V_{L2}}{V_{L1}} = \frac{V_{P2}}{\sqrt{3} V_{P1}} = \frac{1}{\sqrt{3}} \frac{N_2}{N_1}$$

$$\text{Current ratio} = \frac{I_{L2}}{I_{L1}} = \frac{\sqrt{3} I_{P2}}{I_{P1}} = \sqrt{3} \frac{N_1}{N_2}$$

(iv). Δ -Y (Delta star) Connections:

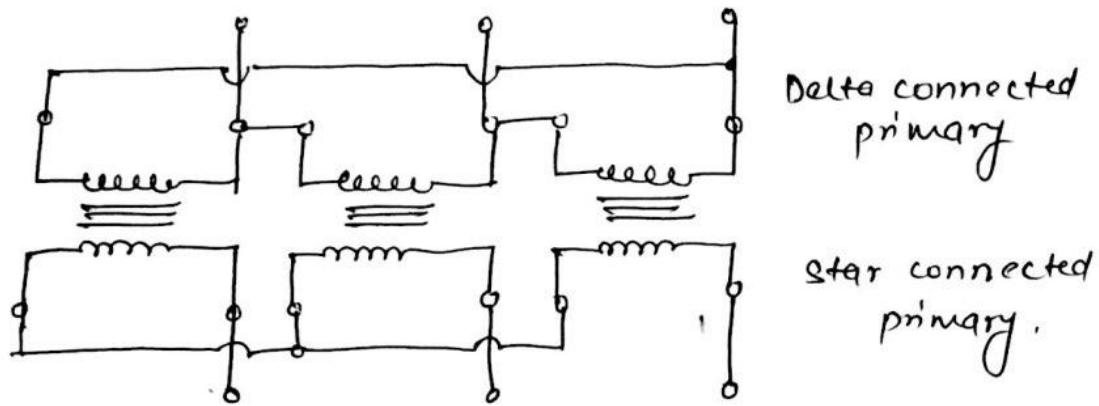

Such connections are used when it is necessary to step up the voltage.

$$\text{Voltage ratio} = \frac{V_{L2}}{V_{L1}} = \frac{\sqrt{3} V_{p2}}{V_{p1}} = \sqrt{3} \frac{N_2}{N_1}$$

$$\text{Current ratio} = \frac{I_{L2}}{I_{L1}} = \frac{I_{p2}}{\sqrt{3} I_{p1}} = \frac{N_1}{\sqrt{3} N_2}$$