

## Single-Phase full converter with RL Load

The operation of converter shown in fig 3(a) can be divided into two identical modes:

Mode 1 when  $T_1$  and  $T_2$  conduct, and mode 2 when  $T_3$  and  $T_4$  conduct. The output current during these modes are similar and we need to consider only one mode to find the output current  $i_L$ .

Mode 1 is valid for  $\alpha \leq \omega t \leq (\pi + \alpha)$ . If  $v_s = V_m \sin \omega t$  or  $v_s = \sqrt{2} V_s \sin \omega t$  is the input voltage, the load current  $i_L$  during mode 1 can be found from

$$L \frac{di_L}{dt} + Ri_L + E = \sqrt{2} V_s \sin \omega t \quad \text{for } i_L \geq 0$$

Solution of this equation

$$i_L = \frac{\sqrt{2} V_s}{Z} \sin(\omega t - \theta) + A_1 e^{-(R/L)t} - \frac{E}{R} \quad \text{for } i_L \geq 0$$

where load impedance  $Z = [R^2 + (\omega L)^2]^{1/2}$  and lead angle  $\theta = \tan^{-1} \frac{\omega L}{R}$ .

Constant  $A_1$  can be determined from initial condition: at  $\omega t = \alpha$ ,  $i_L = I_{L0}$  is found as

$$A_1 = \left[ I_{L0} + \frac{E}{R} - \frac{\sqrt{2} V_s}{Z} \sin(\alpha - \theta) \right] e^{(R/L)(\alpha/\omega)}$$

Substituting  $A_1$  into gives

$$i_L = \frac{\sqrt{2}V_s}{Z} \sin(\omega t - \theta) - \frac{E}{R} + \left[ I_{L0} + \frac{E}{R} - \frac{\sqrt{2}V_s}{Z} \sin(\alpha - \theta) \right] e^{-(R/L)t} \quad (21)$$

At the end of mode-1 in the steady state condition  $i_L(\omega t = \pi + \alpha) = I_L = I_{L0}$ . Applying this condition we get

$$I_{L0} = I_L = \frac{\sqrt{2}V_s}{Z} \frac{-\sin(\alpha - \theta) - \sin(\alpha - \theta) e^{-(R/L)(\pi/\omega)}}{1 - e^{-(R/L)(\pi/\omega)}} - \frac{E}{R} \quad (22)$$

$\text{for } I_{L0} > 0$

The critical value of  $\alpha$  when  $I_{L0}$  becomes zero can be solved for known value of  $\theta$ ,  $R$ ,  $L$ ,  $E$  and  $V_s$  by an iterative method.

rms value <sup>of a thyristor</sup> can be found from eqn. (2)

$$I_R = \left[ \frac{1}{2\pi} \int_{\alpha}^{\pi + \alpha} i_L^2 d(\omega t) \right]^{1/2}$$

r.m.s. output current can be found as

$$I_{rms} = (I_R^2 + I_R^2)^{1/2} = \sqrt{2} I_R$$

Average current of thyristor can be found

$$a) \quad I_A = \frac{1}{2\pi} \int_{\alpha}^{\pi + \alpha} i_L d(\omega t)$$

Average output current can be determined

$$as \quad I_{dc} = I_A + I_A = 2 I_A$$

Discontinuous mode (load current) - The

critical value  $\alpha_c$  at which  $I_{L0}$  becomes zero can be solved. Dividing eq. (22) by  $\sqrt{2}V_s$  and substituting  $R/2 = \cos \alpha$  and  $\omega L = \frac{R}{2}$ , we get

$$0 = \sqrt{2}V_s \frac{Z}{2} \sin(\alpha - \theta) \left[ \frac{1 + e^{-(R/2)(\pi/\omega)}}{1 - e^{-(R/2)(\pi/\omega)}} \right] + E/R$$

which can be solved for critical value of  $\alpha$

$$\alpha_c = \theta - \sin^{-1} \left[ \frac{1 - e^{-(\pi/\omega) R/2}}{1 + e^{-(\pi/\omega) R/2}} \cos \theta \right]$$

where  $x = \frac{\sqrt{2}V_s}{E}$ , is the voltage ratio and  $\theta$  is the load impedance angle for  $\alpha \leq \alpha_c$ ,  $I_{L0} = 0$ . The load current described by eq. (21) flows only during the period  $\alpha \leq \omega t \leq \beta$ . At  $\omega t = \beta$ , the load current falls to zero again.

Note: Varying  $\alpha$  from  $0$  to  $\pi$  can vary the average output voltage from  $\frac{2\sqrt{2}V_m}{\pi}$  to  $-\frac{2\sqrt{2}V_m}{\pi}$ , provided that the load is highly inductive and load current is continuous.

- for a purely resistive load,  $\alpha$  is varies from  $0$  to  $\pi/2$  and the average output voltage vary from  $\frac{2\sqrt{2}V_m}{\pi}$  to  $0$ .

\* The full converter can operate in two quadrants for highly inductive load and operate in one quadrant for a purely resistive load.