 


8254 PIT (PROGRAMMABLE INTERVAL TIMER)

- IC 8254 is used as a device to produce Hardware delays.
- It can also be used to generate a real-time clock, or as a square wave generator etc.
- Hardware delays are more useful than software delays because the μP is not actively involved in producing the delay. Thus when the delay is being produced the μP is free to execute its own program.
- The counting is done using 3 independent 16-bit down counters.
- These counters can take the count in BCD or in Binary.
- After the Counter has finished counting and the required delay is produced, the 8254 interrupts the μP .

Architecture of 8254



The architecture of 8254 can be divided into the following parts:

1) Data Bus Buffer

- This buffer is used to interface the internal data bus with the external (system) data bus.
- It is thus connected to $D_7 - D_0$ from the μP .

2) Read Write Logic

- It accepts the RD & WR signals, which are used to control the flow of data through data bus.
- It also accepts the $A_2 - A_0$ address lines which are used to select one of the Counters or the Control Word as shown below:

A ₁ A ₀	Selection
0 0	Counter 0
0 1	Counter 1
1 0	Counter 2
1 1	Control Word

- It also accepts the CS signal to select the 8254 chip.

3) Control Word Register

SC ₁	SC ₀	RW ₁	RW ₀	M ₂	M ₁	M ₀	BCD
-----------------	-----------------	-----------------	-----------------	----------------	----------------	----------------	-----

SC ₁ SC ₀	Selection
0 0	Select Counter 0
0 1	Select Counter 1
1 0	Select Counter 2
1 1	READ BACK COMMAND (Only for 8254; illegal for 8253)

RW ₁ RW ₀	Selection
0 0	COUNTER LATCH COMMAND
0 1	Read/Write LSB Only
1 0	Read/Write MSB Only
1 1	Read/Write LSB First and then MSB

M ₂ M ₁ M ₀	Mode Selection
0 0 0	Mode 0 --- Interrupt On Terminal Count
0 0 1	Mode 1 --- Monostable Multivibrator
X 1 0	Mode 2 --- Rate Generator
X 1 1	Mode 3 --- Square Wave Generator
1 0 0	Mode 4 --- Software Triggered Strobe
1 0 1	Mode 5 --- Hardware Triggered Strobe

BCD	Type of Count
0	Binary Counter (1 digit → 0H ... FH)
1	BCD Counter (1 digit → 0 ... 9)

- The Control Word Register is an 8-bit register that holds the Control Word as shown above.
- It is selected when A₁ - A₀ contain 11.
- It has a different format when a Read Back command is given for 8254, as shown below

Read Operations

There are 3 ways in which the μP can read the current count:

A) Ordinary Read


- In this method, the counting is stopped by controlling the gate input of a selected counter.
- The Counter is then selected by A₁ - A₀ and IO Read operation is performed.
- First IO Read will give the Lower byte of the Count value, and the second IO Read will give the higher byte.
- The disadvantage here is that counting is disturbed/stopped.

B) Read on Fly

- In this method, the μP reads the count value while the counting is still in progress.
- Thus, it is called as Read On Fly.
- The appropriate value is written in the control word, and IO Read operation is performed.
- The current value of the Count is "latched" internally and returned to the μP .
- The advantage here is that counting is not disturbed.

 
c) Read Back Command

Control Word Register for Read Back Command



- The Read Back Command is available **only** for 8254 and not for 8253.
- The Read Back Command reads the Count value in the **same manner as Read On Fly**.
- In **addition** to the Count, the current Status can **also be latched** using the Read Back command.
- Thus, the appropriate value (for latching the Count and/or Status of the selected counter) is placed in the Control word as shown above.
- The **advantage** here is that the Count and the Status both can be read **without disturbing the counting**.

 Status Word (Status returned after the Read Back Command)



4) 3 Independent Counters

- 8254 has **3 Independent, 16-bit down counters**.
- Each counter can operate have a **Binary or BCD** count.
- Each counter can be in one of the **six possible modes**.
- Each counter can have a max count of $2^{16} = 65535$ i.e. **FFFFH**.
- Each counter has the following signals:
 - i. Clk (Clock Input)
 - ii. Gate (Gate Input)
 - iii. Out (Clock Output)
- The **input clock signal** is applied on the **CLK** line.
- The counter **decrements** the "count value" on **every pulse** of the input clock at **CLK**.
- **When the count becomes zero (Terminal Count i.e. TC), the status of the OUT pin changes.**
This can be used to interrupt the μP .
- The **GATE** pin is used to control the **Counting**.
In most modes, the count value gets **decremented only if the GATE pin is high**.